

THIẾT KẾ HỆ THỐNG SỐ VỚI HDL

BÀI THỰC HÀNH 2

GVHD: Tạ Trí Đức


Sinh viên thực hiện: Phạm Quốc Tiến – 22521472

1) Thiết kế bộ đếm


Code:

```
1  module lab_2_1 (loadEn, clk, load, count);
2  input loadEn, clk;
3  input [2:0] load;
4  output reg [2:0] count;
5  always @ (posedge clk, posedge loadEn)
6  begin
7      if (loadEn)
8          count <= load;
9      else
10         case(count)
11             3'b000 : count <= 3'b110;
12             3'b110 : count <= 3'b100;
13             3'b100 : count <= 3'b111;
14             3'b111 : count <= 3'b011;
15             3'b011 : count <= 3'b000;
16             3'b101 : count <= 3'b010;
17             3'b010 : count <= 3'b111;
18             3'b001 : count <= 3'b110;
19         endcase
20     end
21 endmodule
22
```

RTL:

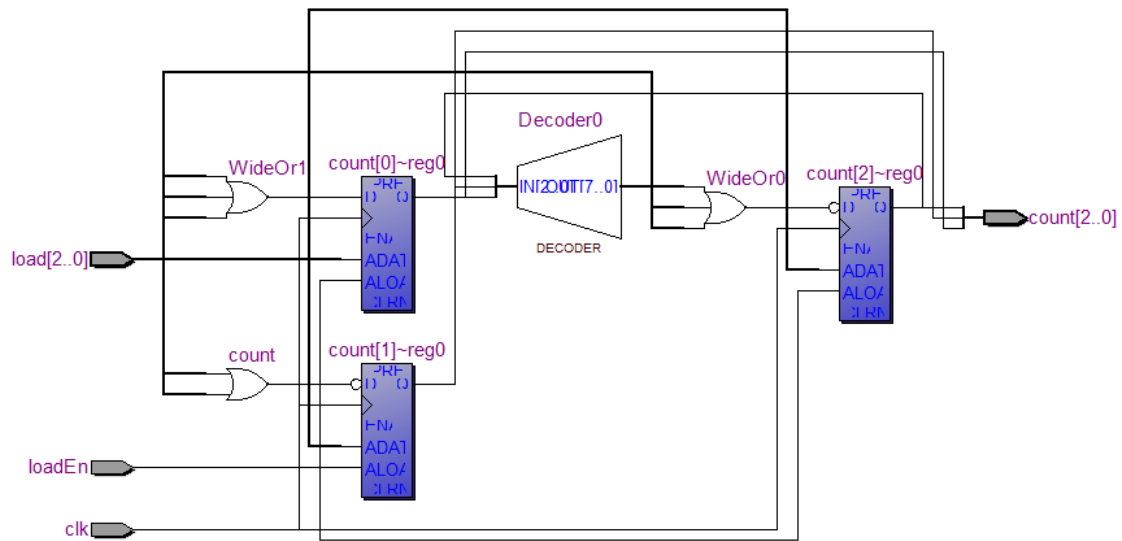

Waveform test function:

 

2) Thiết kế thanh ghi


Code:

```

1 module lab_2_2 (ReadAddress1, ReadAddress2,
2   WriteAddress, WriteData, ReadData1, ReadData2,
3   ReadWriteEn, clk);
4
5   input [4:0] ReadAddress1, ReadAddress2, WriteAddress;
6   input [31:0] WriteData;
7   input ReadWriteEn;
8   input clk;
9   output reg [31:0] ReadData1, ReadData2;
10  reg [31:0] regfile [0:31];
11
12  always @ (posedge clk)
13  begin
14      if (ReadWriteEn)
15      begin
16          regfile[WriteAddress] <= WriteData;
17          ReadData1 <= regfile[ReadAddress1];
18          ReadData2 <= regfile[ReadAddress2];
19      end
20  end
21 endmodule

```

RTL:

 

Waveform test function:

