

THIẾT KẾ HỆ THỐNG SỐ VỚI HDL

BÀI THỰC HÀNH 3

GVHD: Tạ Trí Đức

Sinh viên thực hiện: Phạm Quốc Tiến – 22521472


1) Thiết kế mạch tuần tự

a. Kiểu Moore


Code:

```
1  module moore(input I, clk, output reg Y);
2  reg [1:0] current_state;
3  always @(posedge clk)
4  case(current_state)
5  0 : begin
6      case(I)
7          0: current_state <= 1;
8          1: current_state <= 0;
9      endcase
10     Y <= 0;
11 end
12 1 : begin
13     case(I)
14         0: current_state <= 1;
15         1: current_state <= 2;
16     endcase
17     Y <= 0;
18 end
19 2 : begin
20     case(I)
21         0: current_state <= 3;
22         1: current_state <= 0;
23     endcase
24     Y <= 0;
25 end
26 3 : begin
27     case(I)
28         0: current_state <= 1;
29         1: current_state <= 0;
30     endcase
31     Y <= 1;
32 end
33 endcase
34 endmodule
```


State machine:

 

RTL:

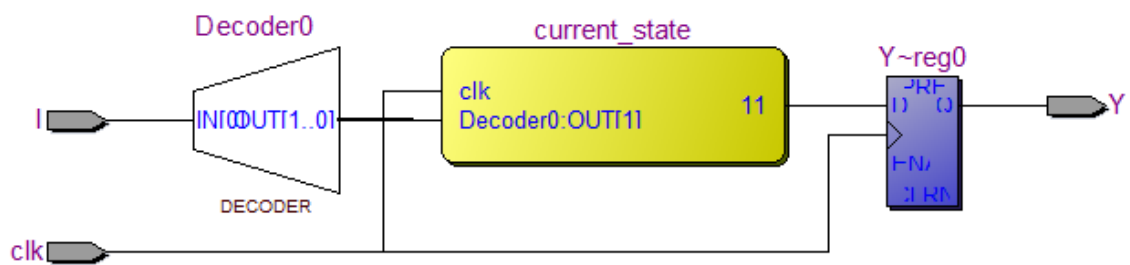

Waveform test function:

 

b. Kiểu Mealy


Code:

```

1  module mealy(input I, clk, output reg Y);
2  reg [1:0] current_state;
3  always @(posedge clk)
4  case(current_state)
5  0 : begin
6      case(I)
7          0: begin current_state <= 1; Y <= 0; end
8          1: begin Y <= 0; end
9      endcase
10 end
11 1 : begin
12     case(I)
13         0: begin current_state <= 1; Y <= 0; end
14         1: begin current_state <= 2; Y <= 0; end
15     endcase
16 end
17 2 : begin
18     case(I)
19         0: begin current_state <= 1; Y <= 1; end
20         1: begin current_state <= 0; Y <= 0; end
21     endcase
22 end
23 endcase
24 endmodule
25

```

RTL:

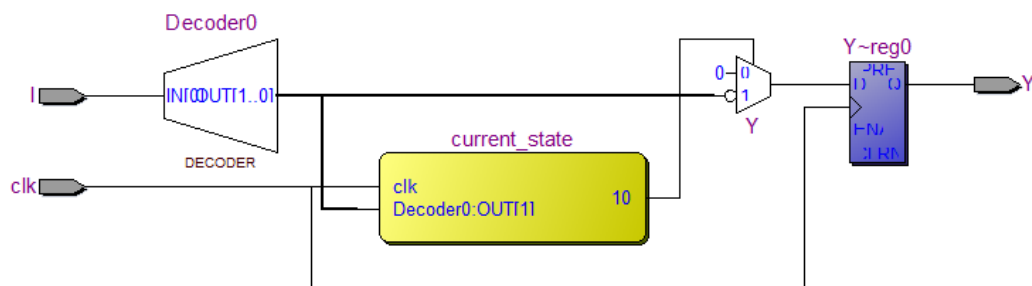

State machine:

